

## **Labs 3 - VHDL Design**



Submitted by **Meldrick Reimmer, Khoi Pham and Selma Boudissa**

## Contents

<b>1</b>	<b>Problem 1</b>	<b>3</b>
<b>2</b>	<b>Problem 2</b>	<b>3</b>
<b>3</b>	<b>Problem 3</b>	<b>4</b>

# 1 Problem 1

```

if (clk 'event and clk='1') then
  -- output the data value at a specific bit
  -- correspond to value of add chosen
  case add is
    when " 0000 " => s <= data (0);
    when " 0001 " => s <= data (1);
    when " 0010 " => s <= data (2);
    when " 0011 " => s <= data (3);
    when " 0100 " => s <= data (4);
    when " 0101 " => s <= data (5);
    when " 0110 " => s <= data (6);
    when " 0111 " => s <= data (7);
    when others => s <= 'Z';
  end case ;
end if;

```

Figure 1: Multiplexer algorithm

The Multiplexer is the algorithm to pick out a bit value of a data pattern correspond to the value of another pattern which we call the data selector



Figure 2: Test bench

**Observation:** Watch the pattern of data "01101001", whenever the clock hit its max, check value of "add" and update value of s proportionally to the bit position of "data". (ie: when add = "0001", get the value of position 2 of data "01101001" which is 0 and assign it to s).


 


Figure 3: Test bench

# 2 Problem 2

 

**Comment:** The 7 segment display is a schematic to run a LED number display system based on a on/off predefined pattern. Notice the letter of the LED that will be used to point to in the program, the schematic algorithm is described as follow.

```

if (clk'event and clk='1') then
  case bcd is
    when "0000" => output7Segment <= "1111110"; -- 'display a led'
    when "0001" => output7Segment <= "1111101"; -- 'display b led'
    when "0010" => output7Segment <= "1111011"; -- 'display c led'
    when "0011" => output7Segment <= "1110111"; -- 'display d led'
    when "0100" => output7Segment <= "1101111"; -- 'display e led'
    when "0101" => output7Segment <= "1011111"; -- 'display f led'
    when "0110" => output7Segment <= "0111111"; -- 'display g led'
  end case;
end if

```

Figure 4: VHDL code

The binary rule in this schematic: "0" will turn on the LED while "1" turns it off. The bits position in 8 bit pattern data correspond to the position of LED "a b c d e f g" that's how this system control the LED display. There is the last bit for the "point" but in 7 segment we don't activate it.


 


Figure 5: Test bench

**Observation:** The pattern of output changes according to the value of bcdcode (every time the clock hit max, ofcourse) followed by the above rule.

### 3 Problem 3

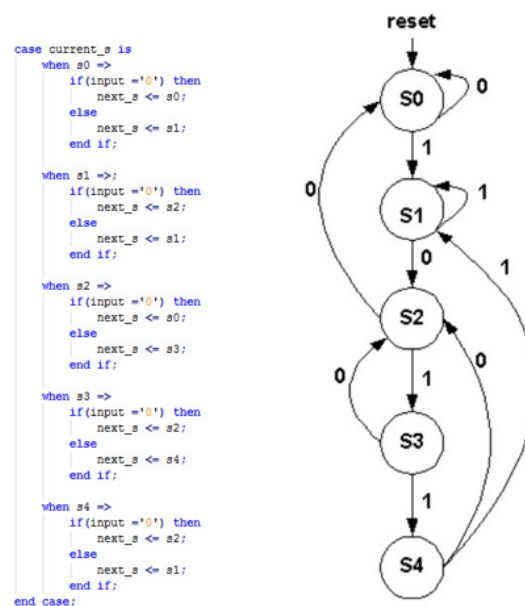

**Observation:** Follow the graph of the exercise, I come up with my state transition program describe as above. The input is the condition for the program to set its next destination state.