

Labs 4 - Test board implementation



Submitted by **Meldrick Reimmer, Khoi Pham and Selma Boudissa**

Contents

1	Problem 1 and 2	3
2	Problem 4	4

1 Problem 1 and 2

Create a design which allows to display a value between 0 and F of one 7 segment Display, and also controllable by the switches on the board: This program is in fact is an advance version of the 7 led display by 7 segment schematic system on Lab 3. I modified it according to the shape of the numbers and letters that will be displayed using these LED components, new schematic is described as followed:

```

if (clk'event and clk='1') then
  case bcd is
    when "0000" => output7Segment <= "0000001"; -- 'display number 0'
    when "0001" => output7Segment <= "1001111"; -- 'display number 1'
    when "0010" => output7Segment <= "0010010"; -- 'display number 2'
    when "0011" => output7Segment <= "0000110"; -- 'display number 3'
    when "0100" => output7Segment <= "1001100"; -- 'display number 4'
    when "0101" => output7Segment <= "0100100"; -- 'display number 5'
    when "0110" => output7Segment <= "0100000"; -- 'display number 6'
    when "0111" => output7Segment <= "0001111"; -- 'display number 7'
    when "1000" => output7Segment <= "0000000"; -- 'display number 8'
    when "1001" => output7Segment <= "0000100"; -- 'display number 9'
    when "1010" => output7Segment <= "0001000"; -- 'display letter A'
    when "1011" => output7Segment <= "0000011"; -- 'display letter B'
    when "1100" => output7Segment <= "1000110"; -- 'display letter C'
    when "1101" => output7Segment <= "0100001"; -- 'display letter D'
    when "1110" => output7Segment <= "0000110"; -- 'display letter E'
    when "1111" => output7Segment <= "0001110"; -- 'display letter F'
    when others => segment7 <= "1111111";
  end case;
end if

```

Figure 1: VHDL Code

Observation The switches on the board handle the signal to pass on the "bcd" port, in order to control the LED to display a particular letter. There will be 4 switches according to 4 bits on the port.

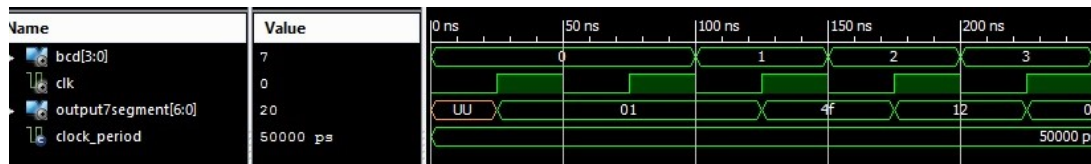


Figure 2: Test bench

Observation: The output7segment get updated its value due proportionally to the value of bcd as described as the rule above. The value here is displayed in hexadecimal mode.

2 Problem 4

The idea is to combine 4 BCD led systems to be able to display not only 0-9 number but from 0-9999.

```
architecture Behavioral of modulo9999 is
begin
    s <= (bcdA * "01")           --multiply by 1
        + (bcdB * "1010")       --multiply by 10
        + (bcdC * "1100100")    --multiply by 100
        + (bcdD * "1111101000"); --multiply by 1000
end Behavioral;
```

Figure 3: VHDL Code

Observation: The algorithm is to sum the 4 digits that generated by 4 BCD led systems with a multiplier of 1,10,100,1000 to get the final 4 digits number (in hexadecimal mode).

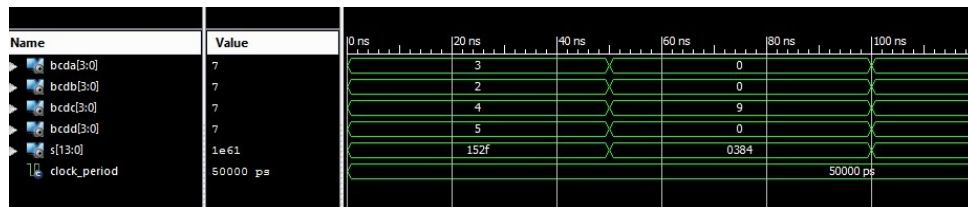


Figure 4: Test bench

Observation: The output s is the computation of $\text{inputA} \times 1 + \text{inputB} \times 10 + \text{inputC} \times 100 + \text{inputD} \times 1000$, but displayed in hexadecimal mode. Ie. Here 152f is the hexadecimal value of 5423 in decimal. And so on, 0384 is hexadecimal value of 900 in decimal.